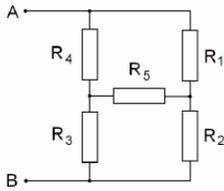
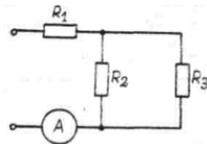
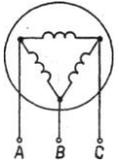
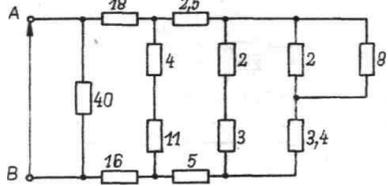
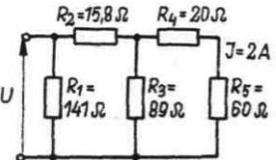
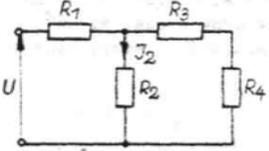
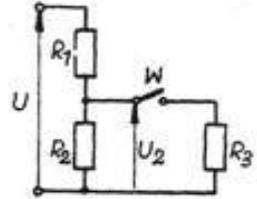




Examination questions from the “Electrical engineering basics” course

Operative level							
Electrical engineering basics							
Questions							
Item	B/D	Question	Correct answer				
1.	B	Ohm’s law for a direct current circuit is as follows: A. $U=R*I$, B. $I=R*U$, C. $R=U*I$, D. $U=R/I$.	<table border="1" style="margin: auto;"> <tr><td style="text-align: center;">A</td></tr> <tr><td style="text-align: center;"> </td></tr> <tr><td style="text-align: center;"> </td></tr> <tr><td style="text-align: center;"> </td></tr> </table>	A			
A							
2.	B	1st Kirchoff’s law for direct current circuits is as follows: A. In a closed circuit, the sum of voltage losses at impedances equals the sum of electromotive forces present in this circuit, B. In a closed circuit, the sum of voltage losses at resistances equals the sum of electromotive forces present in this circuit, C. Algebraic sum of currents in a node equals zero, D. Electric potential difference U between two ends of a conductor is proportional to the intensity and current flowing through a conductor.	<table border="1" style="margin: auto;"> <tr><td style="text-align: center;"> </td></tr> <tr><td style="text-align: center;"> </td></tr> <tr><td style="text-align: center;">C</td></tr> <tr><td style="text-align: center;"> </td></tr> </table>			C	
C							
3.	B	2nd Kirchoff’s law for direct current circuits is as follows: A. In a closed circuit, the sum of voltage losses at impedances equals the sum of electromotive forces present in this circuit, B. The algebraic sum of receiver input voltages in a mesh equals the algebraic sum of source voltages, C. The sum of intensities of currents entering the node equals the sum of current intensities exiting the node, D. Electric potential difference U between two ends of a conductor is proportional to intensity and current flowing through a conductor.	<table border="1" style="margin: auto;"> <tr><td style="text-align: center;"> </td></tr> <tr><td style="text-align: center;">B</td></tr> <tr><td style="text-align: center;"> </td></tr> <tr><td style="text-align: center;"> </td></tr> </table>		B		
B							

4.	D	<p>Equivalent resistance between points A and B of a circuit shown in the picture equals:</p>  <p>A. 2.5 Ω, B. 10 Ω, C. 5 Ω, D. 3 Ω,</p> <p>Given: $R_1=3 \Omega$, $R_2=2 \Omega$, $R_3=2 \Omega$, $R_4=3 \Omega$, $R_5=4 \Omega$</p>	<table border="1" style="width: 100%; height: 100%;"> <tr><td style="text-align: center;">A</td></tr> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td> </td></tr> </table>	A			
A							
5.	B	<p>The principle of superposition can be explained as follows:</p> <p>A. In a series circuit, drops of voltage caused by individual energy sources operating individually may be replaced with a single drop of voltage, B. The response of a linear circuit to simultaneous action of several stimuli equals the sum of responses for each stimulus individually, C. All voltage sources in a circuit may be replaced by a gap, D. All current sources in a circuit may be replaced by a contact,</p>	<table border="1" style="width: 100%; height: 100%;"> <tr><td> </td></tr> <tr><td style="text-align: center;">B</td></tr> <tr><td> </td></tr> <tr><td> </td></tr> </table>		B		
B							
6.	D	<p>Find voltage drops in specific circuit branches in the picture, if the ammeter indicates 3 A.</p> <p>Given: $R_1=3 \Omega$, $R_2=2 \Omega$, $R_3=4 \Omega$.</p> <p>A. 8 V, 4 V, 4 V, B. 5 V, 6 V, 6 V, C. 9 V, 4 V, 4 V, D. 4 V, 5 V, 5 V.</p> 	<table border="1" style="width: 100%; height: 100%;"> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td style="text-align: center;">C</td></tr> <tr><td> </td></tr> </table>			C	
C							

7.	D	<p>Three identical stator windings of a three phase motor were connected into a delta. Resistance measured between terminals A and B equals 44Ω. Resistance of a single winding equals:</p> <p>A. 22Ω, B. 44Ω, C. 66Ω, D. 55Ω,</p> 	<table border="1" style="width: 100%; height: 100%; text-align: center;"> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td>C</td></tr> <tr><td> </td></tr> </table>			C	
C							
8.	D	<p>The circuit described in the picture is supplied from a direct voltage source of value $U = 220 \text{ V}$. The numbers denote resistance in ohms. Current received from the source equals:</p> <p>A. 1 A, B. 11 A, C. 2 A, D. 20 A.</p> 	<table border="1" style="width: 100%; height: 100%; text-align: center;"> <tr><td> </td></tr> <tr><td>B</td></tr> <tr><td> </td></tr> <tr><td> </td></tr> </table>		B		
B							
9.	D	<p>In a passive circuit there are given resistances and the current flowing through resistance R_4. Supply voltage equals:</p> <p>A. 110 V, B. 220 V, C. 311 V, D. 440 V.</p> 	<table border="1" style="width: 100%; height: 100%; text-align: center;"> <tr><td> </td></tr> <tr><td>B</td></tr> <tr><td> </td></tr> <tr><td> </td></tr> </table>		B		
B							

10.	D	<p>In a circuit presented in the picture, the current intensity $I_2=2$ A. Resistance values: $R_1 = 3 \Omega$, $R_2 = 18 \Omega$, $R_3 = 3 \Omega$, $R_4 = 6 \Omega$. Equivalent resistance of the circuit and supply voltage equal:</p> <p>A. $10 \Omega, 72$ V, B. $9 \Omega, 54$ V, C. $11 \Omega, 36$ V, D. $15 \Omega, 41$ V.</p> 	<table border="1" style="width: 100%; height: 100%; text-align: center;"> <tr><td> </td></tr> <tr><td>B</td></tr> <tr><td> </td></tr> <tr><td> </td></tr> </table>		B		
B							
11.	D	<p>Voltage divider made up of R_1 and R_2 resistors was supplied with voltage of $U = 200$ V.</p>  <p>Given: $R_1 = 100 \Omega$, $R_2 = R_3 = 300 \Omega$. Voltage values U_2 at the output of the divider with open and closed W switch equal:</p> <p>A. 150 V, 120 V, B. 100 V, 200 V, C. 210 V, 115 V, D. 200 V, 175 V.</p>	<table border="1" style="width: 100%; height: 100%; text-align: center;"> <tr><td>A</td></tr> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td> </td></tr> </table>	A			
A							

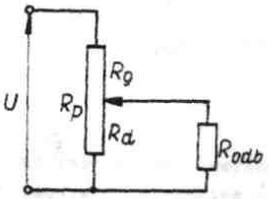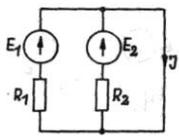12.	D	<p>Electrical load with resistance of $R_{odb} = 40 \Omega$ is supplied from a potentiometer ($R_p = 80 \Omega$), whose terminals are connected to voltage of $U = 120V$</p>  <p>Values of electrical load current and voltage, assuming the potentiometer slider is in the middle position ($R_g = R_d$) are equal to:</p> <p>A. 10 V, 5 A, B. 15 V, 2 A, C. 40 V, 1 A, D. 35 V, 5 A.</p>	<table border="1" style="margin-left: auto; margin-right: auto;"> <tbody> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td style="text-align: center;">C</td></tr> <tr><td> </td></tr> </tbody> </table>			C	
C							
13.	D	<p>In a circuit presented in the picture, electromotive forces equal $E_1 = 100 V$, $E_2 = 120 V$, resistances $R_1 = 10 \Omega$, $R_2 = 40 \Omega$.</p>  <p>Current I has the following value:</p> <p>A. 10 A, B. 13 A, C. 15 A, D. 25 A.</p>	<table border="1" style="margin-left: auto; margin-right: auto;"> <tbody> <tr><td> </td></tr> <tr><td style="text-align: center;">B</td></tr> <tr><td> </td></tr> </tbody> </table>		B		
B							
14.	B	<p>Coulomb's law can be written using the following formula:</p> <p>A. $F = k \frac{Q_1 Q_2}{r^2}$,</p>	<table border="1" style="margin-left: auto; margin-right: auto;"> <tbody> <tr><td style="text-align: center;">A</td></tr> <tr><td> </td></tr> </tbody> </table>	A			
A							

		<p>B. $F = k \frac{r_1 r_2}{Q^2}$,</p> <p>C. $F = r^2 Q_1 Q_2$,</p> <p>$F = k \frac{U}{d}$.</p> <p>D.</p>	<input type="checkbox"/> <input type="checkbox"/>
15.	B	<p>Value of electric field intensity in a given point is determined by the following function:</p> <p>A. $E = \frac{F}{q}$,</p> <p>B. $F = \frac{E}{q}$,</p> <p>C. $E = \frac{q}{F}$,</p> <p>D. $C = \frac{F}{q}$.</p>	<input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/>
16.	B	<p>Equivalent capacity Cz for two condensers with capacities of C1 and C2 in a parallel connection may be calculated using the formula</p> <p>A. $Cz = 1/C1 + 1/C2$,</p> <p>B. $1/Cz = 1/C1 + 1/C2$,</p> <p>C. $Cz = C1 + C2$,</p> <p>D. $Cz = (C1 + C2) / C1 * C2$.</p>	<input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/>
17.	B	<p>What is the average rectified value of sinusoidal alternating voltage in volts:</p> <p>A. 2π,</p> <p>B. 314,</p> <p>C. 0,</p> <p>D. 230.</p>	<input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/>
18.	B	<p>Which formula presents the true function between the maximum and RMS value for sinusoidal alternating voltage?</p> <p>A. $U_m = 0.707 U$,</p> <p>B. $U = 0.707 U_m$,</p>	<input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/>

		<p>C. $U = \sqrt{2} U_m$,</p> <p>D. $U = \sqrt{3} U_m$.</p>	<input type="text"/>
19.	B	<p>For network frequency of $f = 50$ Hz, the period equals:</p> <p>A. 5 ms,</p> <p>B. 10 ms,</p> <p>C. 20 ms,</p> <p>D. 30 ms.</p>	<input type="text"/> <input type="text"/> <input type="text"/> C <input type="text"/> <input type="text"/>
20.	B	<p>Pulsation is described by the following function:</p> <p>A. $2 \pi T$,</p> <p>B. $2 \pi f$,</p> <p>C. $f \pi / 2$,</p> <p>D. $\sqrt{2} f$.</p>	<input type="text"/> <input type="text"/> B <input type="text"/> <input type="text"/> <input type="text"/>
21.	B	<p>The phase shift between voltage and current in a given electrical load is the name for:</p> <p>A. the difference of initial phases of voltage and current,</p> <p>B. the difference of initial phases of voltages in a circuit,</p> <p>C. the quotient of initial phases of voltage and current,</p> <p>D. the product of initial phases of voltage and current.</p>	<input type="text"/> A <input type="text"/> <input type="text"/> <input type="text"/> <input type="text"/>
22.	B	<p>For a resistance electrical load in a sinusoidal alternating current circuit, the phase shift angle between current and voltage equals:</p> <p>A. 180°,</p> <p>B. 90°,</p> <p>C. 0°,</p> <p>D. -90°.</p>	<input type="text"/> <input type="text"/> <input type="text"/> C <input type="text"/> <input type="text"/>


23.	B	<p>For a load with ideal inductance in a sinusoidal alternating current circuit, the phase shift angle between current and voltage equals:</p> <p>A. 180° (output voltage “leads” the current), B. -180° (voltage “lags” in relation to the current), C. 90° (output voltage “leads” the current), D. -90° (voltage “lags” in relation to the current),</p>	<div style="border: 1px solid black; padding: 5px; text-align: center;"> <input type="text"/> <input type="text"/> <input type="text"/> <input type="text"/> </div>
24.	B	<p>The unit for impedance is a:</p> <p>A. siemens [S], B. henry [H], C. ohm [Ω], D. farad [F].</p>	<div style="border: 1px solid black; padding: 5px; text-align: center;"> <input type="text"/> <input type="text"/> <input type="text"/> <input type="text"/> </div>
25.	B	<p>The unit for inductive reactance is a:</p> <p>A. siemens [S], B. henry [H], C. ohm [Ω], D. farad [F].</p>	<div style="border: 1px solid black; padding: 5px; text-align: center;"> <input type="text"/> <input type="text"/> <input type="text"/> <input type="text"/> </div>
26.	B	<p>Capacitive reactance is expressed by the following function:</p> <p>A. $X_c = \frac{1}{\omega C}$, B. $X_c = \omega C$, C. $Z_c = R_c + X_c$, D. $Z_c = X_c$.</p>	<div style="border: 1px solid black; padding: 5px; text-align: center;"> <input type="text"/> <input type="text"/> <input type="text"/> <input type="text"/> </div>
27.	B	<p>Inductive reactance is expressed by the following function:</p> <p>A. $X_L = \omega L$, B. $X_L = \frac{1}{\omega L}$, C. $Z_L = R_L + X_L$, D. $Z_L = X_L$.</p>	<div style="border: 1px solid black; padding: 5px; text-align: center;"> <input type="text"/> <input type="text"/> <input type="text"/> <input type="text"/> </div>
28.	B	<p>For a sinusoidal alternating circuit with a real induction coil load the following function used to determine impedance is true:</p>	<div style="border: 1px solid black; padding: 5px; text-align: center;"> <input type="text"/> </div>

		<p>A. $Z_L = R_L - X_L$,</p> <p>B. $Z_L = R_L + X_L$,</p> <p>C. $Z_L = R_L^2 + X_L^2$,</p> <p>D. $Z_L = \sqrt{R_L^2 + X_L^2}$.</p>	<table border="1"> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td>D</td></tr> </table>			D	
D							
29.	D	<p>How many times is the RMS value of full-wave rectified sinusoidal waveform greater than the RMS value of this voltage before rectification?</p> <p>A. two times,</p> <p>B. square root times,</p> <p>C. two times smaller,</p> <p>D. it is the same.</p>	<table border="1"> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td>D</td></tr> </table>				D
D							
30.	D	<p>What shall be the impedance of the Z_o electric load supplied from a real voltage source with intrinsic impedance of $Z_w = R_w + jX_w$ so that it operates (Z_o) at a maximum active power (maximum power transfer condition)</p> <p>A. $Z_o = R_w$,</p> <p>B. $Z_o = X_w$,</p> <p>C. $Z_o = R + jX_w$,</p> <p>D. $Z_o = R - jX_w$.</p>	<table border="1"> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td>D</td></tr> </table>				D
D							
31.	D	<p>Current and voltage have the following waveforms: $u = 310\sin(\omega t)$, $i = 2\sin(\omega t - \pi/4)$. Instantaneous voltage and current values for $t = 0.005s$, provided $f = 50$ Hz, equal approximately:</p> <p>A. $u = 230$ V, $i = 1.7$ A,</p> <p>B. $u = 360$ V, $i = 2.2$ A,</p> <p>C. $u = 310$ V, $i = 1.4$ A,</p> <p>D. $u = 110$ V, $i = 3.3$ A.</p>	<table border="1"> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td>C</td></tr> <tr><td> </td></tr> </table>			C	
C							
32.	D	<p>Two sinusoidal alternating values have a phase shift angle of $\varphi = \pi/6$. What is the time shift of their positive maximum values if frequency equals $f = 500$ Hz.</p> <p>A. $166.7 \mu s$,</p> <p>B. 20 ms,</p> <p>C. $10 \mu s$,</p> <p>D. $311 \mu s$.</p>	<table border="1"> <tr><td>A</td></tr> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td> </td></tr> </table>	A			
A							
33.	D	<p>Indication of a volt meter connected to the network with a sinusoidal voltage equals 230 V. Maximum voltage value is approximately equal to:</p> <p>A. 440 V,</p> <p>B. 380 V,</p>	<table border="1"> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td>C</td></tr> <tr><td> </td></tr> </table>			C	
C							

		C. 325 V, D. 311 V.	
34.	D	Current with a waveform of $i = I_m \sin(\omega t + 2\pi/3)$ s measured with an electromagnetic ammeter. What is the indication of the ammeter if at the moment of $t = 0$ the instantaneous current value is $i = 1.3$ A. A. 2.12 A, B. 1.06 A, C. 1.49 A, D. 3.00 A.	<input type="checkbox"/> B <input type="checkbox"/>
35.	B	The unit of active power is A. VA, B. W, C. var, D. Vs.	<input type="checkbox"/> B <input type="checkbox"/>
36.	B	The unit of passive power is A. VA, B. W, C. var, D. J.	<input type="checkbox"/> C <input type="checkbox"/>
37.	B	Apparent power is expressed by the following function: A. $S = \sqrt{P+Q}$, B. $S = \sqrt{P^2 + Q^2}$, C. $S = P + Q$, D. $S = P \cdot Q$.	<input type="checkbox"/> B <input type="checkbox"/>
38.	B	Active power in a single phase circuit with a resistant-inductive electrical load is specified by the following function: A. $U \cdot I \cdot \text{tg}\phi$, B. $U \cdot I \cdot \sin\phi$, C. $U \cdot I \cdot \cos\phi$, D. $U \cdot I$.	<input type="checkbox"/> C <input type="checkbox"/>
39.	B	Resonance frequency in a series RLC circuit can be presented by the following function:	<input type="checkbox"/>

		<p>A. $f = \sqrt{L^2 + C^2}$,</p> <p>B. $f = \frac{1}{2\pi \cdot \sqrt{L \cdot C}}$,</p> <p>C. $f = \frac{1}{2\pi \cdot \sqrt{R \cdot L \cdot C}}$,</p> <p>D. $f = \frac{1}{\sqrt{L \cdot C}}$.</p>	<table border="1"> <tr><td>B</td></tr> <tr><td> </td></tr> <tr><td> </td></tr> </table>	B			
B							
40.	B	<p>Resonance frequency in a parallel RLC circuit can be presented by the following function:</p> <p>A. $f = \sqrt{L^2 + C^2}$,</p> <p>B. $f = \frac{1}{2\pi \cdot \sqrt{L \cdot C}}$,</p> <p>C. $f = \frac{1}{\sqrt{L \cdot C}}$,</p> <p>D. $f = \frac{1}{2\pi \cdot \sqrt{R \cdot L \cdot C}}$.</p>	<table border="1"> <tr><td> </td></tr> <tr><td>B</td></tr> <tr><td> </td></tr> <tr><td> </td></tr> </table>		B		
B							
41.	D	<p>An ideal coil with inductance of $L = 86 \text{ mH}$ was connected to a sinusoidal current source of voltage $U = 220 \text{ V}$ (RMS value) and frequency of $f = 50 \text{ Hz}$. The values of current flowing through the coil (RMS value), the passive, active and apparent power consumed by the coil equal:</p> <p>A. $I = 8.15 \text{ A}$, $P = 0 \text{ W}$, $Q = 1793 \text{ var}$, $S = 1793 \text{ VA}$,</p> <p>B. $I = 8.15 \text{ A}$, $P = 1793 \text{ W}$, $Q = 0 \text{ var}$, $S = 1793 \text{ VA}$,</p> <p>C. $I = 8.15 \text{ A}$, $P = 0 \text{ W}$, $Q = 1793 \text{ var}$, $S = 0 \text{ VA}$,</p> <p>D. $I = 8.15 \text{ A}$, $P = 1793 \text{ W}$, $Q = 1793 \text{ var}$, $S = 0 \text{ VA}$.</p>	<table border="1"> <tr><td>A</td></tr> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td> </td></tr> </table>	A			
A							
42.	D	<p>An ideal capacitor with capacity of $C = 36.7 \text{ }\mu\text{F}$ was connected to a sinusoidal current network of voltage $U = 380 \text{ V}$ and frequency of $f = 50 \text{ Hz}$. The value of current flowing through a condenser, apparent, active and passive power consumed by the condenser equal:</p> <p>A. $I = 4.38 \text{ A}$, $P = 1664 \text{ W}$, $Q = 0 \text{ var}$, $S = 1664 \text{ VA}$,</p> <p>B. $I = 4.38 \text{ A}$, $P = 0 \text{ W}$, $Q = -1664 \text{ var}$, $S = 1664 \text{ VA}$,</p> <p>C. $I = 4.38 \text{ A}$, $P = 1664 \text{ W}$, $Q = 1664 \text{ var}$, $S = 1664 \text{ VA}$,</p> <p>D. $I = 0 \text{ A}$, $P = 1664 \text{ W}$, $Q = 0 \text{ var}$, $S = 1664 \text{ VA}$.</p>	<table border="1"> <tr><td> </td></tr> <tr><td>B</td></tr> <tr><td> </td></tr> <tr><td> </td></tr> </table>		B		
B							
43.	D	<p>Coil with a resistance of $R = 80 \text{ }\Omega$ and inductance of $L = 255 \text{ mH}$ was connected to a source of sinusoidal current with voltage of $U = 24 \text{ V}$ and frequency of $f = 50 \text{ Hz}$. The value of current in the circuit, voltages at the U_R resistance and voltage at inductive reactance U_L equal respectively:</p>	<table border="1"> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td> </td></tr> </table>				

		<p>A. $I = 0.08 \text{ A}$, $U_R = 5 \text{ V}$, $U_L = 5 \text{ V}$, B. $I = 0.33 \text{ A}$, $U_R = 25 \text{ V}$, $U_L = 27 \text{ V}$, C. $I = 0.12 \text{ A}$, $U_R = 13 \text{ V}$, $U_L = 11 \text{ V}$, D. $I = 0.21 \text{ A}$, $U_R = 17 \text{ V}$, $U_L = 17 \text{ V}$.</p>	D
44.	D	<p>In a coreless coil connected to a power source with direct voltage of $U = 4.2 \text{ V}$, there is a current flow of $I = 0.14 \text{ A}$, and when it is connected to a sinusoidal voltage power source ($U = 75 \text{ V}$ $f = 50 \text{ Hz}$), the current in the coil is $I = 1.5 \text{ A}$. Inductive reactance and inductance of the coil and the power received from the network with direct and alternating current equal respectively:</p> <p>A. $X_L = 40 \text{ } \Omega$, $L = 0.127 \text{ H}$, $P_+ = 0.59 \text{ W}$, $P_- = 67.5 \text{ W}$, B. $X_L = 50 \text{ } \Omega$, $L = 0.16 \text{ H}$, $P_+ = 0.12 \text{ W}$, $P_- = 32.4 \text{ W}$, C. $X_L = 10 \text{ } \Omega$, $L = 0.21 \text{ H}$, $P_+ = 0.32 \text{ W}$, $P_- = 32.0 \text{ W}$, D. $X_L = 20 \text{ } \Omega$, $L = 0.41 \text{ H}$, $P_+ = 0.52 \text{ W}$, $P_- = 12.0 \text{ W}$.</p>	A
45.	D	<p>After connecting a coil with a steel core to a source with voltage of $U = 120 \text{ V}$ and frequency of $f = 100 \text{ Hz}$ the current in the coil was equal to 0.5 A. After the core was remove from the coil, current increased to 8 A. Coil resistance $R = 4 \text{ } \Omega$. Inductance of the coil in both cases, not taking into account energy losses in the core, equals approximately:</p> <p>A. $L_1 = 0.80 \text{ H}$, $L_2 = 0.2 \text{ H}$, B. $L_1 = 0.54 \text{ H}$, $L_2 = 0.01 \text{ H}$, C. $L_1 = 0.38 \text{ H}$, $L_2 = 0.02 \text{ H}$, D. $L_1 = 0.12 \text{ H}$, $L_2 = 0.12 \text{ H}$.</p>	C

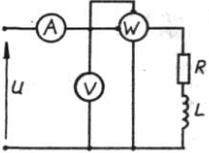46.	D	<p>In order to calculate induction coil parameters. it was connected, along with meters, to a network with sinusoidal voltage and frequency of $f = 50 \text{ Hz}$. Meters indicated the following values: voltmeter $U = 220 \text{ V}$, ammeter $I = 5.3 \text{ A}$, wattmeter $P = 780 \text{ W}$. The manner of connecting the meters is presented in drawing 11. Parameters of the coil (R, L, Z) are respectively:</p> <p>A. $R = 98 \ \Omega$, $L = 27.8 \text{ mH}$, $Z = 41.5 \ \Omega$, B. $R = 27.8 \ \Omega$, $L = 98 \text{ mH}$, $Z = 41.5 \ \Omega$, C. $R = 41.5 \ \Omega$, $L = 98 \text{ mH}$, $Z = 27.8 \ \Omega$, D. $R = 41.5 \ \Omega$, $L = 27.8 \text{ mH}$, $Z = 41.5 \ \Omega$.</p> 	<table border="1" style="width: 100%; height: 100%; text-align: center;"> <tr><td> </td></tr> <tr><td>B</td></tr> <tr><td> </td></tr> <tr><td> </td></tr> </table>		B		
B							
47.	D	<p>Condenser with capacity of $C = 10 \ \mu\text{F}$ was connected in series with a resistor with resistance of $R = 500 \ \Omega$ and included in an alternating voltage network with an RMS voltage of $U = 240 \text{ V}$. Current in a circuit and drops of U_R, U_C voltages equal respectively:</p> <p>A. $I = 0.21 \text{ A}$, $U_R = 200 \text{ V}$, $U_C = 100 \text{ V}$, B. $I = 0.33 \text{ A}$, $U_R = 202.5 \text{ V}$, $U_C = 128.8 \text{ V}$, C. $I = 0.51 \text{ A}$, $U_R = 220.5 \text{ V}$, $U_C = 118.8 \text{ V}$, D. $I = 0.41 \text{ A}$, $U_R = 202.5 \text{ V}$, $U_C = 128.8 \text{ V}$.</p>	<table border="1" style="width: 100%; height: 100%; text-align: center;"> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td>D</td></tr> </table>				D
D							
48.	D	<p>A condenser was included in series with a heater with power $P = 40 \text{ W}$ and rated voltage of $U = 220 \text{ V}$. What shall be the approximate condenser capacitance value so that after connecting the voltage of $U = 380 \text{ V}$ to a two-terminal circuit, the voltage at the heater was equal to 220 V ($f = 50 \text{ Hz}$).</p> <p>A. $C = 1.87 \ \mu\text{F}$, B. $C = 18.7 \ \mu\text{F}$, C. $C = 1.87 \ \text{mF}$, D. $C = 18.7 \ \text{mF}$.</p>	<table border="1" style="width: 100%; height: 100%; text-align: center;"> <tr><td>A</td></tr> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td> </td></tr> </table>	A			
A							

49.	B	<p>In a three-phase symmetrical system all voltages have the same RMS and the shift angle between voltages of specific phases equals:</p> <p>A. 30°, B. 60°, C. 90°, D. 120°.</p>	<table border="1" style="width: 100%; height: 100%; text-align: center;"> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td>D</td></tr> </table>				D
D							
50.	B	<p>In three-phase systems there are phase values of I_f, U_f and line values I, U, depending on whether the three phase system is arranged in a star, or a delta. In a star network, the following functions are true:</p> <p>A. $I_f = \sqrt{3}I$ and $U_f = \sqrt{3}U$, B. $I_f = I$ and $U_f = \frac{U}{\sqrt{3}}$, C. $I_f = \frac{I}{\sqrt{3}}$ and $U_f = U$, D. $I_f = I$ and $U_f = \sqrt{3}U$.</p>	<table border="1" style="width: 100%; height: 100%; text-align: center;"> <tr><td> </td></tr> <tr><td>B</td></tr> <tr><td> </td></tr> </table>		B		
B							
51.	B	<p>In a positive star network, the line voltage leads the phase voltage by a phase angle equal:</p> <p>A. 30°, B. 45°, C. 120°, D. 90°.</p>	<table border="1" style="width: 100%; height: 100%; text-align: center;"> <tr><td>A</td></tr> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td> </td></tr> </table>	A			
A							
52.	B	<p>In three-phase systems there are phase values of I_f, U_f and line values I, U, depending on whether the symmetrical three-phase system is arranged in a star, or a delta. In a delta network, the following functions are true:</p> <p>A. $I_f = \sqrt{3}I$ and $U_f = \sqrt{3}U$, B. $I_f = I$ and $U_f = \frac{U}{\sqrt{3}}$, C. $I_f = \sqrt{3}I$ and $U_f = \sqrt{3}U$, D. $I_f = \frac{I}{\sqrt{3}}$ and $U_f = U$.</p>	<table border="1" style="width: 100%; height: 100%; text-align: center;"> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td>D</td></tr> </table>				D
D							
53.	B	<p>Active power received by a three-phase symmetric load with given phase values is expressed by the following function:</p> <p>A. $P = \sqrt{3} U_f I_f \cos \varphi$, B. $P = 3U_f I_f \cos \varphi$,</p>	<table border="1" style="width: 100%; height: 100%; text-align: center;"> <tr><td> </td></tr> <tr><td>B</td></tr> <tr><td> </td></tr> </table>		B		
B							


		<p>C. $P = \sqrt{3} U_f \sqrt{3} I_f \cos \varphi$,</p> <p>D. $P = \sqrt{3} U_f I_f$.</p>	<input type="text"/>
54.	B	<p>Passive power received by a three-phase symmetric load with given phase values is expressed by the following function:</p> <p>A. $Q = \sqrt{3} U_f I_f \sin \varphi$,</p> <p>B. $Q = 3U_f I_f$,</p> <p>C. $Q = 3U_f 3I_f \sin \varphi$,</p> <p>D. $Q = 3U_f I_f \sin \varphi$.</p>	<input type="text"/> <input type="text"/> <input type="text"/> <input type="text"/> D
55.	B	<p>Active power received by a three-phase symmetric load with given line values is expressed by the following function:</p> <p>A. $P = \sqrt{3} U I$,</p> <p>B. $P = 3U I \cos \varphi$,</p> <p>C. $P = \sqrt{3} U \sqrt{3} I \cos \varphi$,</p> <p>D. $P = \sqrt{3} U I \cos \varphi$.</p>	<input type="text"/> <input type="text"/> <input type="text"/> <input type="text"/> D
56.	B	<p>Apparent power received by a three-phase symmetric load with given line values is expressed by the following function:</p> <p>A. $S = \sqrt{3} U I$,</p> <p>B. $S = 3U I \cos \varphi$,</p> <p>C. $S = \sqrt{3} U \sqrt{3} I \cos \varphi$,</p> <p>D. $S = \sqrt{3} U I \cos \varphi$.</p>	<input type="text"/> A <input type="text"/> <input type="text"/> <input type="text"/>
57.	B	<p>The sum of instantaneous electromotoric forces in a symmetrical three-phase circuit is equal to:</p> <p>A. 120 V,</p> <p>B. 400 V,</p> <p>C. 0 V,</p> <p>D. 230 V.</p>	<input type="text"/> <input type="text"/> <input type="text"/> C <input type="text"/>
58.	B	<p>Transformation of a single branch of a star circuit into a delta has the following form:</p> <p>A. $Z_{12} = Z_1 + Z_3 + \frac{Z_1}{Z_3}$,</p> <p>B. $Z_{12} = Z_1 + Z_2 + \frac{Z_1 \cdot Z_2}{Z_3}$,</p>	<input type="text"/> <input type="text"/> B <input type="text"/> <input type="text"/>

		$C. \quad Z_1 = \frac{Z_{12} \cdot Z_{13}}{Z_{12} + Z_{13} + Z_{23}},$ $D. \quad Z_3 = \frac{Z_{23} \cdot Z_{13}}{Z_{12} + Z_{13} + Z_{23}}.$					
59.	B	<p>RMS value of a periodic function has the following form:</p> $A. \quad A = \sqrt{\frac{1}{T} \int_0^T f(t) dt},$ $B. \quad A = \sqrt{\frac{1}{T} f^2(t)},$ $C. \quad A = \frac{1}{T} \sqrt{\int_0^T f^2(t) dt},$ $D. \quad A = \sqrt{\frac{1}{T} \int_0^T f^2(t) dt}.$	<table border="1"> <tbody> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td>D</td></tr> </tbody> </table>				D
D							
60.	B	<p>Assuming the amplitude of kth harmonic number is represented as A_{m_k}, the RMS of kth harmonic number is expressed by the following function:</p> $A. \quad A_k = \sqrt{2} \cdot A_{m_k},$ $B. \quad A_k = \frac{A_{m_k}}{\sqrt{2}},$ $C. \quad A_k = \sqrt{2} \cdot A_{m_k}^2,$ $D. \quad A_k = A_{m_k}^2.$	<table border="1"> <tbody> <tr><td> </td></tr> <tr><td>B</td></tr> <tr><td> </td></tr> <tr><td> </td></tr> </tbody> </table>		B		
B							

61.	B	<p>Assuming the amplitude of kth harmonic number is represented as A_{m_k} and A_0 is a constant component, the RMS value of the f(t) function is expressed by the following function:</p> <p>A. $A_{sk} = \sqrt{A_0 + \sum_{k=1}^{\infty} A_{m_k}}$,</p> <p>B. $A_{sk} = \sqrt{A_0^2 + \sum_{k=1}^{\infty} A_{m_k}^2}$,</p> <p>C. $A_{sk} = \sqrt{\sum_{k=1}^{\infty} A_{m_k}^2}$,</p> <p>D. $A_{sk} = \sqrt{A_0 + \sum_{k=1}^{\infty} A_{m_k}^2}$.</p>	<table border="1" style="margin-left: auto; margin-right: auto;"> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td style="text-align: center;">B</td></tr> <tr><td> </td></tr> </table>			B	
B							
62.	B	<p>Average rectified value of the f(t) function is defined as:</p> <p>A. $A_0 = \frac{1}{T} \int_0^T f(t) dt$,</p> <p>B. $A_0 = \frac{1}{T} \int_0^T \sqrt{f(t)} dt$,</p> <p>C. $A_0 = \frac{1}{T} \int_0^T f^2(t) dt$,</p> <p>D. $A_0 = \frac{1}{T} \int_0^T \sqrt{f^2(t)} dt$.</p>	<table border="1" style="margin-left: auto; margin-right: auto;"> <tr><td style="text-align: center;">A</td></tr> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td> </td></tr> </table>	A			
A							

63.	B	<p>Sine wave peak factor $s = \frac{A_{\max}}{A_{sk}}$ equals:</p> <p>A. $\frac{\sqrt{3}}{2}$,</p> <p>B. $\frac{\sqrt{3}}{2}$,</p> <p>C. $\frac{\sqrt{2}}{2}$,</p> <p>D. $\frac{\sqrt{2}}{2}$.</p>	<table border="1"> <tbody> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td>C</td></tr> <tr><td> </td></tr> </tbody> </table>			C	
C							
64.	B	<p>Determining RMS value for specific harmonic waveforms as A_k, the total distortion factor h is expressed by the following function:</p> <p>A. $h = \frac{\sqrt{ A_2 + A_3 + \dots}}{\sqrt{ A_1 + A_2 + A_3 + \dots}}$,</p> <p>B. $h = \frac{\sqrt{ A_2 ^2 + A_3 ^2 + \dots}}{\sqrt{ A_1 ^2 + A_2 ^2 + A_3 ^2 + \dots}}$,</p> <p>C. $h = \frac{\sqrt{ A_2 ^2 + A_3 ^2 + \dots}}{\sqrt{ A_1 ^2 + A_2 ^2 + A_3 ^2 + \dots}}$,</p> <p>D. $h = \frac{\sqrt{(A_2 + A_3 + \dots)^2}}{\sqrt{(A_1 + A_2 + A_3 + \dots)^2}}$.</p>	<table border="1"> <tbody> <tr><td> </td></tr> <tr><td>B</td></tr> <tr><td> </td></tr> <tr><td> </td></tr> </tbody> </table>		B		
B							

65.	B	<p>Total harmonic distortion is defined using the following dependence:</p> <p>A. $h = \frac{A_1^2}{\sqrt{A_0^2 + A_1^2 + A_2^2 + \dots}},$</p> <p>B. $h = \sqrt{\frac{A_1}{A_0^2 + A_1^2 + A_2^2 + \dots}},$</p> <p>C. $h = \frac{A_1}{A_0^2 + A_1^2 + A_2^2 + \dots},$</p> <p>D. $h = \frac{\sqrt{A_2^2 + A_3^2 + A_4^2 + \dots}}{A_1}.$</p>	<div style="border: 1px solid black; width: 40px; height: 40px; margin: 0 auto; text-align: center; line-height: 40px;">D</div>
66.	B	<p>If the RMS value of the 1st harmonics waveform is defined as A_1, and the RMS value of kth harmonics is defined as A_k, the total distortion of the kth harmonics is defined using a function:</p> <p>A. $h_k = \sqrt{\frac{ A_k }{ A_1 }} \cdot 100\%,$</p> <p>B. $h_k = \left(\frac{ A_k }{ A_1 }\right)^2 \cdot 100\%,$</p> <p>C. $h_k = \frac{ A_k }{ A_1 } \cdot 100\%,$</p> <p>D. $h_k = \frac{ A_k ^2}{ A_1 } \cdot 100\%.$</p>	<div style="border: 1px solid black; width: 40px; height: 40px; margin: 0 auto; text-align: center; line-height: 40px;">C</div>
67.	B	<p>The reversibility condition of a two-port network for ABCD chain parameters is as follows:</p> <p>A. $AD - BC = 1,$</p> <p>B. $AD + BC = 1,$</p> <p>C. $AD \cdot BC = 1,$</p> <p>D. $AD / BC = 1.$</p>	<div style="border: 1px solid black; width: 40px; height: 40px; margin: 0 auto; text-align: center; line-height: 40px;">A</div>
68.	B	<p>Which equation is true in the case of a symmetric two-port network for ABCD chain parameters:</p>	<div style="border: 1px solid black; width: 40px; height: 20px; margin: 0 auto;"></div>

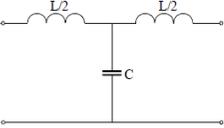		<p>A. $AD = BD$, B. $AD = BC$, C. $A = B$, D. $A = D$.</p>	<input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> D
69.	B	<p>A two-port network is called active if:</p> <p>A. there are uncompensated energy sources inside, B. It fulfils the reciprocity principle, e.g. line passive two-port network, C. swapping input and output terminals does not change the currents and voltages in the remaining part of the circuit which includes a two-port network, D. At least one two-port network element is non-linear.</p>	<input type="checkbox"/> A <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/>
70.	B	<p>The passband edge is a frequency for which the voltage amplification of the filter:</p> <p>A. decreases by 10 dB, B. increases by 3 dB, C. decreases by 3 dB, D. decreases by 6 dB,</p>	<input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> C <input type="checkbox"/>
71.	B	<p>The filter presented in the picture is of the following filter type:</p> <p>A. low-pass, B. band-pass, C. high-pass, D. band-stop.</p> 	<input type="checkbox"/> A <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/>
72.	B	<p>Intrinsic inductance of the coil L is defined by a formula:</p> <p>A. $L = B \cdot q \cdot v$, B. $L = \Phi \cdot i$, C. $L = N \cdot \Phi \cdot i$, D. $L = N \cdot \Phi / i$.</p>	<input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> D
73.	B	<p>The units of magnetic field strength and inductance are:</p> <p>A. henry, tesla, B. weber, tesla, C. A/m, tesla,</p>	<input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> C

		D. A*m, weber.	
74.	B	The unit of electric field intensity is: A. V*m, B. A*m, C. VA/m, D. V/m.	<input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> D
75.	B	Direction and sense of force $F=B*i*L$ can be determined based on: A. Coulomb's law, B. left hand rule, C. right hand rule, D. Ohm's law.	<input type="checkbox"/> <input type="checkbox"/> B <input type="checkbox"/> <input type="checkbox"/>
76.	B	Sense of electromotoric force $e=B*i*v$ may be determined based on: A. the Coulomb's law, B. left hand rule, C. right hand rule, D. Ohm's law.	<input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> C <input type="checkbox"/>
77.	B	Magnetic permeability is divided by μ_0 it is a number smaller than 1 for the following material types: A. paramagnetic, B. diamagnetic, C. ferromagnetic, D. isotropic.	<input type="checkbox"/> <input type="checkbox"/> B <input type="checkbox"/> <input type="checkbox"/>
78.	B	Magnetic induction is a value: A. that describes the operation of the condenser, B. that describes the magnetic field, C. of magnetic permeability, D. of current intensity.	<input type="checkbox"/> <input type="checkbox"/> B <input type="checkbox"/> <input type="checkbox"/>
79.	B	Condenser capacity is calculated from the following formula: A. $C=I*R$, B. $C=U/I$, C. $C=Q/I$, D. $C=Q/U$.	<input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> D
80.	B	Low value of $\cos\phi$ depends on: A. Inclusion of large heating elements, B. High active energy consumption, C. High passive energy consumption, D. Generator efficiency.	<input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> C <input type="checkbox"/>

81.	B	The value of $\cos\phi$ may be increased by: A. decreasing passive energy consumption, B. increasing passive energy consumption, C. decreasing power of generators, D. increasing power of generators,	<table border="1"><tr><td data-bbox="1877 209 1968 240">A</td></tr><tr><td data-bbox="1877 240 1968 272"> </td></tr><tr><td data-bbox="1877 272 1968 304"> </td></tr><tr><td data-bbox="1877 304 1968 336"> </td></tr></table>	A			
A							