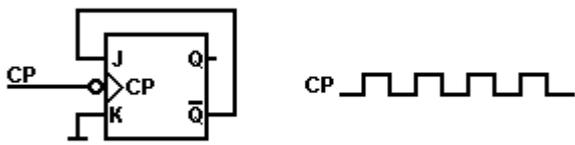
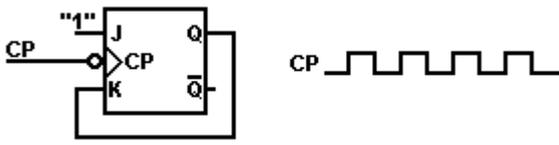


## Examination questions on the subject of Digital Technology


Operational level							
Digital Technology							
<b>Questions</b>							
O/T - means Basic/Advanced							
Item	O/T	Question	Correct answer				
1.	O	<p>The JK flip flop switch has been connected according to the shown diagram, assuming that it was zeroed at the initial moment..</p>  <p>System</p> <ol style="list-style-type: none"> <li>modifies its state after each steep sloping clock slope,</li> <li>maintains the previous condition,</li> <li>switches to state 0 and remains there,</li> <li>switches to state 1 and remains there.</li> </ol>	<table border="1" style="margin: auto;"> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td style="text-align: center;">D</td></tr> </table>				D
D							
2.	O	<p>The JK flip flop switch has been connected according to the shown diagram, assuming that it was zeroed at the initial moment..</p>  <p>System</p> <ol style="list-style-type: none"> <li>changes its condition after each descending clock slope,</li> <li>maintains the previous condition,</li> <li>switches to state 0 and remains there,</li> <li>switches to state 1 and remains there.</li> </ol>	<table border="1" style="margin: auto;"> <tr><td style="text-align: center;">A</td></tr> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td> </td></tr> </table>	A			
A							
3.	O	<p>Examine a system that performs the following logical function:</p> $Y(d, c, b, a) = \Sigma (5, 10, 11, 13, 14, 15).$ <p>In the system structure, in order to eliminate the possibility of static hazard, the following additional components should be introduced</p> <ol style="list-style-type: none"> <li><math>d \bar{c} a</math>,</li> <li><math>\bar{d} c a</math>,</li> <li><math>d \bar{c} \bar{a}</math>,</li> </ol>	<table border="1" style="margin: auto;"> <tr><td style="text-align: center;">A</td></tr> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td> </td></tr> </table>	A			
A							

d)  $d \ c \ \bar{a}$

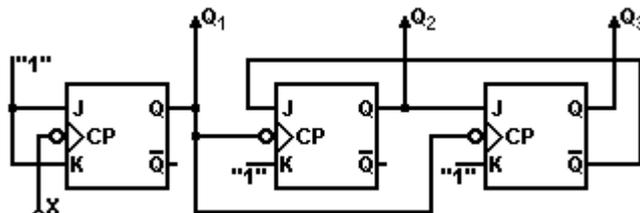4.

○

Assume that  $Q_1(0) = Q_2(0) = Q_3(0) = 0$ , with  $Q_1, Q_2, Q_3$  having weights of 2<sup>0</sup>, 2<sup>1</sup>, 2<sup>2</sup> respectively. The system shown in the figure is:




- a) the answers b, c, d are not true,
- b) the forward counting modulo 7 counter,
- c) the forward counting in the natural binary code modulo 6 counter.,
- d) the forward counting in the natural binary code modulo 5 counter.

C

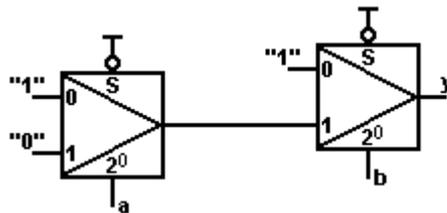5.



○



What function does the system illustrated in the figure perform?




- a) the answers b, c, d are not true,
- b) NAND,
- c) XNOR,
- d) XOR.

B

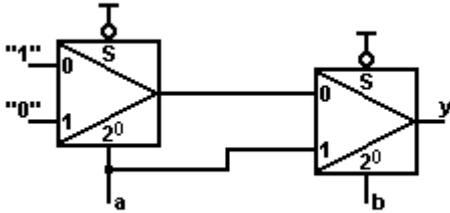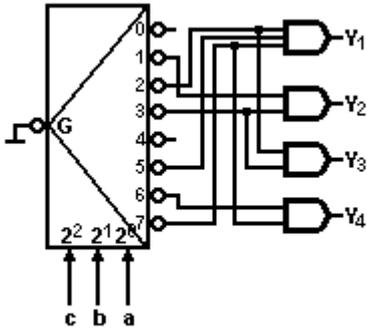
6.	○	<p>What function does the system illustrated in the figure perform?</p>  <p>a) NAND, b) NOR, c) XNOR, d) XOR.</p>	<table border="1" data-bbox="1268 246 1364 380"> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td>C</td></tr> <tr><td> </td></tr> </table>			C	
C							
7.	○	<p>What function does the system illustrated in the figure perform?</p>  <p>a) <math>Y_1(a, b, c) = \Pi(2,5,7)</math>, <math>Y_2(c, b, a) = \Pi(1,3)</math>,  <math>Y_3(a, b, c) = \Pi(2,3)</math>, <math>Y_4(c, b, a) = \Pi(6,5)</math>,  b) <math>Y_1(c, b, a) = \Pi(2,5,7)</math>, <math>Y_2(c, b, a) = \Pi(1,3)</math>,  <math>Y_3(c, b, a) = \Pi(2,3)</math>, <math>Y_4(c, b, a) = \Pi(6,5)</math>.  c) <math>Y_1(c, b, a) = \Pi(2,5,7)</math>, <math>Y_2(c, b, a) = \Pi(1,3)</math>,  <math>Y_3(c, b, a) = \Pi(2,3)</math>, <math>Y_4(a, b, c) = \Pi(6,5)</math>.</p>	<table border="1" data-bbox="1268 739 1364 873"> <tr><td> </td></tr> <tr><td>B</td></tr> <tr><td> </td></tr> <tr><td> </td></tr> </table>		B		
B							

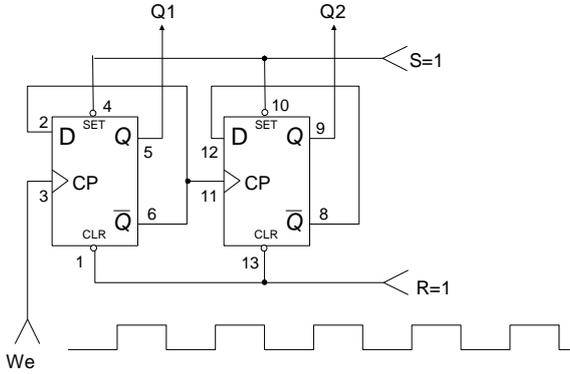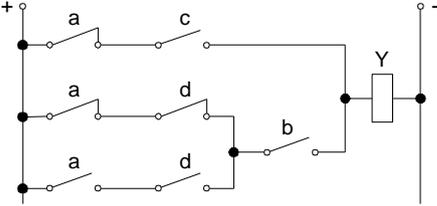8.	○	<p>Assume that <math>Q1(0) = Q2(0) = 0</math>, with <math>Q1, Q2</math> having weights of 20.21 respectively. The system shown in the figure is:</p>  <p>a) the backwards counting in the natural binary code modulo 4 counter,  b) the forward counting in the natural binary code modulo 4 counter,  c) the forward counting in the natural binary code modulo 3 counter.</p>	<table border="1" data-bbox="1267 315 1366 412"> <tr><td> </td></tr> <tr><td>B</td></tr> <tr><td> </td></tr> </table>		B	
B						
9.	○	<p>Specify the Y function of the contact system</p>  <p>a) <math>\bar{a}c + (\bar{a}\bar{d} + a\bar{d})bc</math>,  b) <math>\bar{a}c + (\bar{a}\bar{d} + a\bar{d})c</math>,  c) <math>\bar{a}c + (\bar{a}\bar{d} + a\bar{d})b</math>.</p>	<table border="1" data-bbox="1267 1182 1366 1279"> <tr><td> </td></tr> <tr><td>C</td></tr> <tr><td> </td></tr> </table>		C	
C						
10.	○	<p>Determine the signal at the y output.</p>	<table border="1" data-bbox="1267 1787 1366 1883"> <tr><td> </td></tr> <tr><td>C</td></tr> <tr><td> </td></tr> </table>		C	
C						

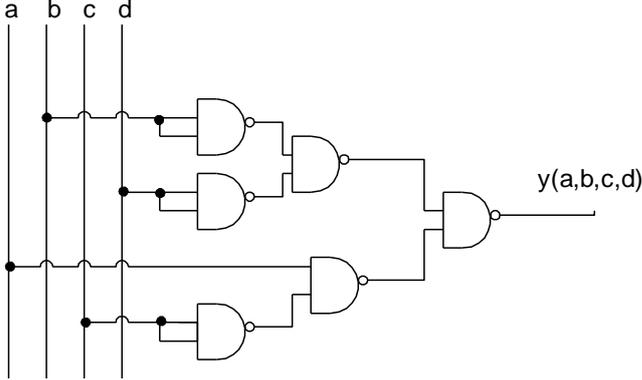		 <p>a) <math>\bar{b} d + \bar{a} c</math>,  b) <math>b \bar{d} + \bar{a} c</math>,  c) <math>b \bar{d} + a \bar{c}</math>.</p>				
11.	<input type="radio"/>	<p>In the architecture of PLA, the matrix of products and sums meets the following conditions</p> <p>a) the products is programmable, the sums is programmed permanently,  b) both matrices are programmable,  c) sums is programmable, the products are programmed permanently.</p>	<table border="1" style="width: 100px; height: 40px; text-align: center;"> <tr><td> </td></tr> <tr><td>B</td></tr> <tr><td> </td></tr> </table>		B	
B						
12.	<input type="radio"/>	<p>The number <math>46_{10}</math> in the hexadecimal code should be recorded as</p> <p>a) 3 E H,  b) 2 F H,  c) 2 E H.</p>	<table border="1" style="width: 100px; height: 40px; text-align: center;"> <tr><td> </td></tr> <tr><td>C</td></tr> <tr><td> </td></tr> </table>		C	
C						
13.	<input type="radio"/>	<p>The number <math>378_{10}</math> in the BCD code is recorded as</p> <p>a) ( 0011 0111 1010)<sub>BCD</sub>,  b) ( 0011 0111 1000)<sub>BCD</sub>,  c) ( 0111 0011 1000)<sub>BCD</sub>.</p>	<table border="1" style="width: 100px; height: 40px; text-align: center;"> <tr><td> </td></tr> <tr><td>B</td></tr> <tr><td> </td></tr> </table>		B	
B						
14.	<input type="radio"/>	<p>The sum of the numbers <math>10111011_2</math> and <math>10111_2</math> shall be as follow</p> <p>a) <math>11110010_2</math>,  b) <math>11010010_2</math>,  c) <math>10110010_2</math>.</p>	<table border="1" style="width: 100px; height: 40px; text-align: center;"> <tr><td> </td></tr> <tr><td>B</td></tr> <tr><td> </td></tr> </table>		B	
B						

15.	○	<p>The number <math>+21_{10}</math> in 8-bit code completion to 2 (U2) should be written as</p> <p>a) 00010101 <math>U_2</math>,</p> <p>b) 10010101 <math>U_2</math>,</p> <p>c) 00110101 <math>U_2</math>.</p>	<table border="1" style="margin-left: auto; margin-right: auto;"> <tr><td style="text-align: center;">A</td></tr> <tr><td> </td></tr> <tr><td> </td></tr> </table>	A		
A						
16.	○	<p>The number <math>+21_{10}</math> in 8-bit code module character (ZM) is written as</p> <p>a) 00010101 <math>ZM</math>,</p> <p>b) 10010101 <math>ZM</math>,</p> <p>c) 00110101 <math>ZM</math>.</p>	<table border="1" style="margin-left: auto; margin-right: auto;"> <tr><td style="text-align: center;">A</td></tr> <tr><td> </td></tr> <tr><td> </td></tr> </table>	A		
A						
17.	○	<p>The number <math>+21_{10}</math> in 8-bit code of the completion code up to 1 (U1) is written as</p> <p>a) 00010101 <math>U_1</math>,</p> <p>b) 10010101 <math>U_1</math>,</p> <p>c) 00110101 <math>U_1</math>.</p>	<table border="1" style="margin-left: auto; margin-right: auto;"> <tr><td style="text-align: center;">A</td></tr> <tr><td> </td></tr> <tr><td> </td></tr> </table>	A		
A						
18.	○	<p>The function performed by the EXCLUSIVE OR (EX OR) 2-way gateway can be written as</p> <p>a) <math>Y=f(a, b) = a + b</math></p> <p>b) <math>Y=f(a, b) = a\bar{b} + \bar{a}b</math></p> <p>c) <math>Y=f(a, b) = \bar{a}\bar{b} + ab</math></p>	<table border="1" style="margin-left: auto; margin-right: auto;"> <tr><td> </td></tr> <tr><td style="text-align: center;">B</td></tr> <tr><td> </td></tr> </table>		B	
B						
19.	○	<p>The function performed by the EXCLUSIVE OR (EX OR) 2-way gateway can be written as</p> <p>a) <math>Y=f(a, b) = \overline{a \oplus b}</math></p> <p>b) <math>Y=f(a, b) = a \oplus b = a \otimes b</math></p> <p>c) <math>Y=f(a, b) = a \oplus b = \overline{a \otimes b}</math></p>	<table border="1" style="margin-left: auto; margin-right: auto;"> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td style="text-align: center;">C</td></tr> </table>			C
C						
20.	○	<p>The function performed by the EXCLUSIVE NOR (EX NOR) 2-input gateway can be written as</p> <p>a) <math>Y=f(a, b) = a + b</math></p> <p>b) <math>Y=f(a, b) = a\bar{b} + \bar{a}b</math></p> <p>c) <math>Y=f(a, b) = \bar{a}\bar{b} + ab</math></p>	<table border="1" style="margin-left: auto; margin-right: auto;"> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td style="text-align: center;">C</td></tr> </table>			C
C						


21.	○	<p>What role does the system with the following symbol play</p> <p style="text-align: center;">74154N</p> <p>a) demultiplexer with 4 address inputs, at the output 0 is active,  b) demultiplexer with 4 address inputs, at the output 1 is active,  c) multiplexer with 4 address inputs.</p>	<table border="1" style="margin-left: auto; margin-right: auto;"> <tr><td style="text-align: center;">A</td></tr> <tr><td> </td></tr> <tr><td> </td></tr> </table>	A			
A							
22.	○	<p>What does the system with the following symbol contain</p> <p style="text-align: center;">74153N</p> <p>a) 2 multiplexers, each with its own 4 information inputs and 2 address inputs,  b) 2 multiplexers with 4 information inputs and 2 shared address inputs,  c) 2 demultiplexers with 4 address inputs.</p>	<table border="1" style="margin-left: auto; margin-right: auto;"> <tr><td> </td></tr> <tr><td style="text-align: center;">B</td></tr> <tr><td> </td></tr> </table>		B		
B							
23.	○	<p>The EXCLUSIVE OR (EX OR) gateway is represented by the following symbol</p> <p>a)  ,  b)  ,  c)  ,  d)  .</p>	<table border="1" style="margin-left: auto; margin-right: auto;"> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td style="text-align: center;">C</td></tr> <tr><td> </td></tr> </table>			C	
C							

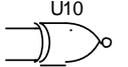24.	○	<p>The NOR gateway is represented by the following symbol</p> <p>a) U5A  7400N ,</p> <p>b) U7A  7402N ,</p> <p>c) U9A  7486N ,</p> <p>d) U10 </p>	<table border="1" data-bbox="1268 224 1364 347"> <tr><td> </td></tr> <tr><td>B</td></tr> <tr><td> </td></tr> <tr><td> </td></tr> </table>		B		
B							
25.	○	<p>The following environment is used to prepare digital control algorithms for PLD programmable systems</p> <p>a) BASCOM, b) Delphi, c) Max Plus Baseline and Quartus.</p>	<table border="1" data-bbox="1268 974 1364 1075"> <tr><td> </td></tr> <tr><td> </td></tr> <tr><td>C</td></tr> </table>			C	
C							
26.	○	<p>In PAL architecture, the matrix of the product and sum fulfills the following conditions</p> <p>a) the products is programmable, the sums is programmed permanently, b) both matrices are programmable, c) sums is programmable, the products are pre-programmed permanently.</p>	<table border="1" data-bbox="1268 1310 1364 1411"> <tr><td>A</td></tr> <tr><td> </td></tr> <tr><td> </td></tr> </table>	A			
A							

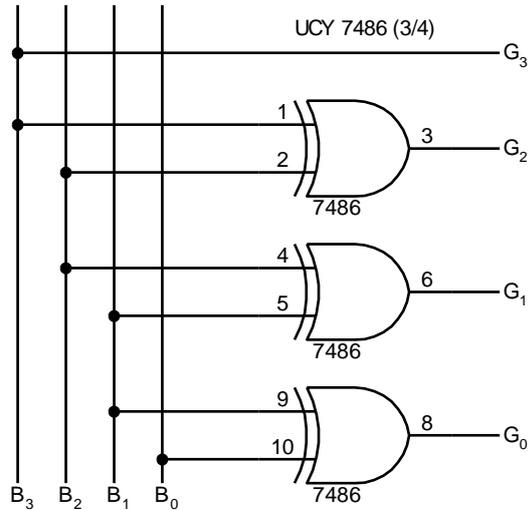27.

O

The figure shows a diagram of the 4-bit natural binary code translator to the Gray code.



Determine the signal at the outputs of the circuits  $G_3, G_2, G_1, G_0$  when the signal 1 0 0 0 1 is given on the inputs  $B_3, B_2, B_1, B_0$  respectively.


- a) 1 0 0 1,
- b) 1 0 1 1,
- c) 1 0 0 1,
- d) 1 1 0 1.

D

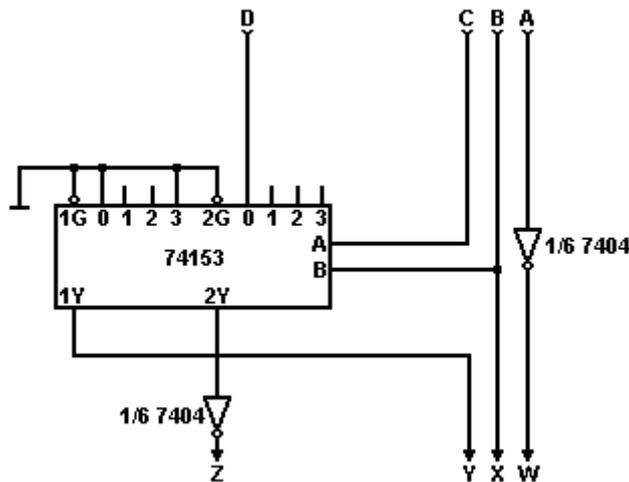28.

O

Inputs D, C, B, A have the following weights: 8,4,4,2,1 respectively, whereas addresses inputs A, B of UCY 74153 multiplexer have the following weights: 1,2 respectively.



Determine the signal at the circuit output when the input D, C, C, B, A is given a signal of 1 0 0 0 0.

- a) 1 0 0 1,
- b) 1 0 1 1,
- c) 0 0 0 1,
- d) 1 1 0 1.

C